

ECE 448

Lecture 7

VGA Display Part 1

Required Reading

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 12, VGA Controller I: Graphic
- *Source Codes of Examples*
http://academic.csuohio.edu/chu_p/rtl/fpga_vhdl.html
- *Nexys3 Reference Manual*
VGA Port, pages 15-17

Basics



High Performance

CoolClock

Low Power

DataCatcher


VGA – Video Graphics Array

- Video display standard introduced in the late 1980's
- Widely supported by PC graphics hardware and monitors
- Used initially with the CRT (cathode ray tube) monitors
- Later adopted for LCD monitors as well


VGA – Characteristic Features

- Resolution: 640x480
- Display: up to 256 colors (8 bits)
- Refresh Rate: 25Hz, 30Hz, 60Hz (frames / second)
- RGB: Red, Green and Blue analog signals


Operation of a CRT monitor

 


CRT Monitor – Conceptual Diagram

 

CRT Monitor – Scanning Pattern

 

CRT Monitor – Horizontal Scan

 

VGA Controller




High Performance

CoolClock

Low Power

DataCache

VGA Controller – Simplified View

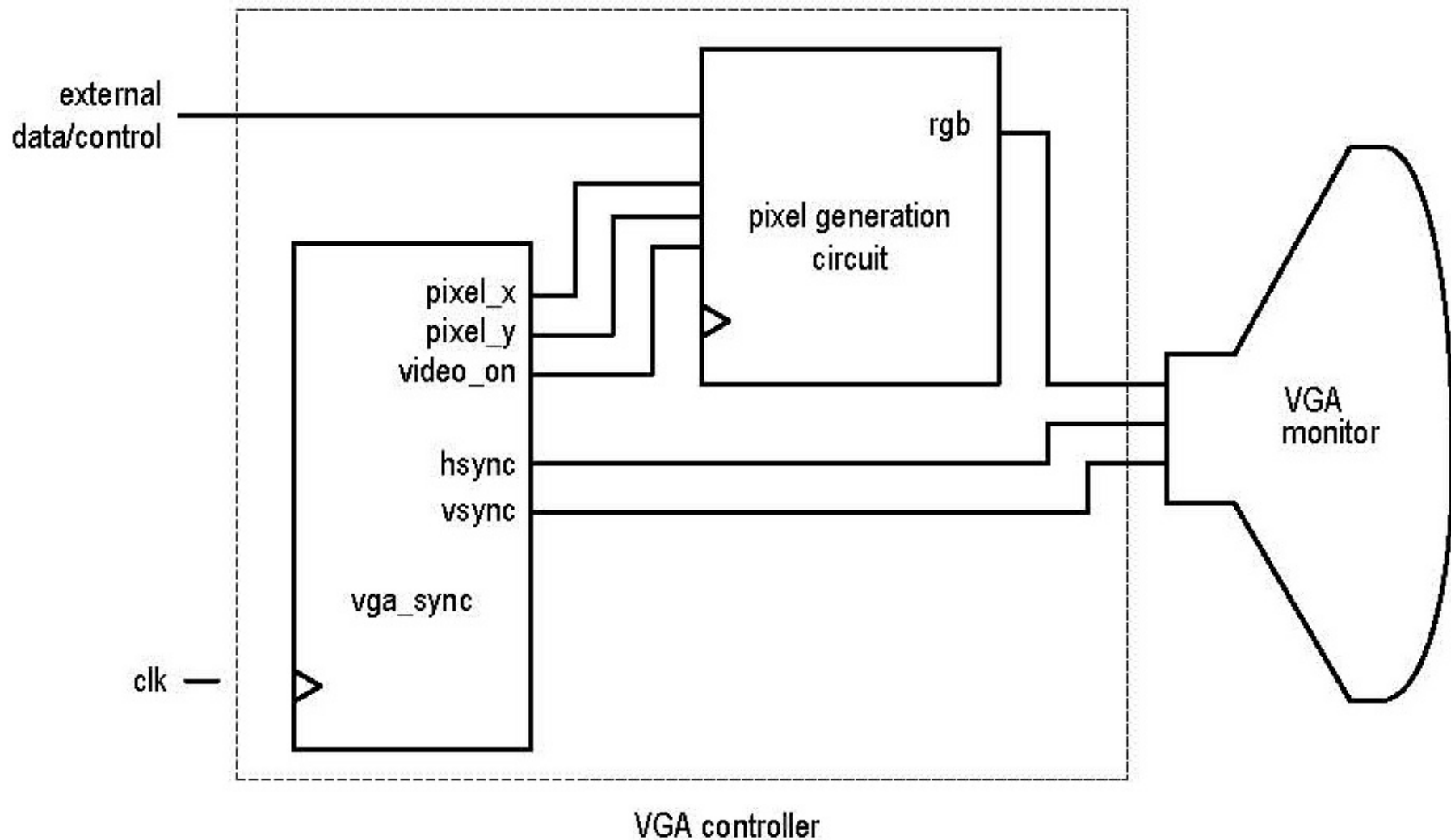

Three-bit VGA Color Combinations

Red (R)	Green (G)	Blue (B)	Resulting color
0	0	0	black
0	0	1	blue
0	1	0	green
0	1	1	cyan
1	0	0	red
1	0	1	magenta
1	1	0	yellow
1	1	1	white

VGA Synchronization




High Performance

CoolClock

Low Power

DataCache


Horizontal Synchronization

 

Four regions of hsync

- Display: 0..639, width = 640
- Right border (front porch): 640..655, width = 16
- Retrace (horizontal flyback): 656..751, width=96
- Left border (back porch): 752..799, width=48

Vertical Synchronization

 


Four regions of vsync

- Display: 0..479, width = 480 lines
- Bottom border (front porch): 480..489, width = 10
- Retrace (vertical flyback): 490..491, width=2
- Top border (back porch): 491..524, width=33

Pixel Rate

- p : the number of pixels in a horizontal scan line
 $p = 800$ pixels/line
- l : the number of horizontal lines in a screen
 $l = 525$ lines/screen
- s : the number of screens per second (refresh rate)
 $s = 60$ screens/second

$$\text{Pixel Rate} = p \cdot l \cdot s = 25 \text{ Mpixels/second}$$

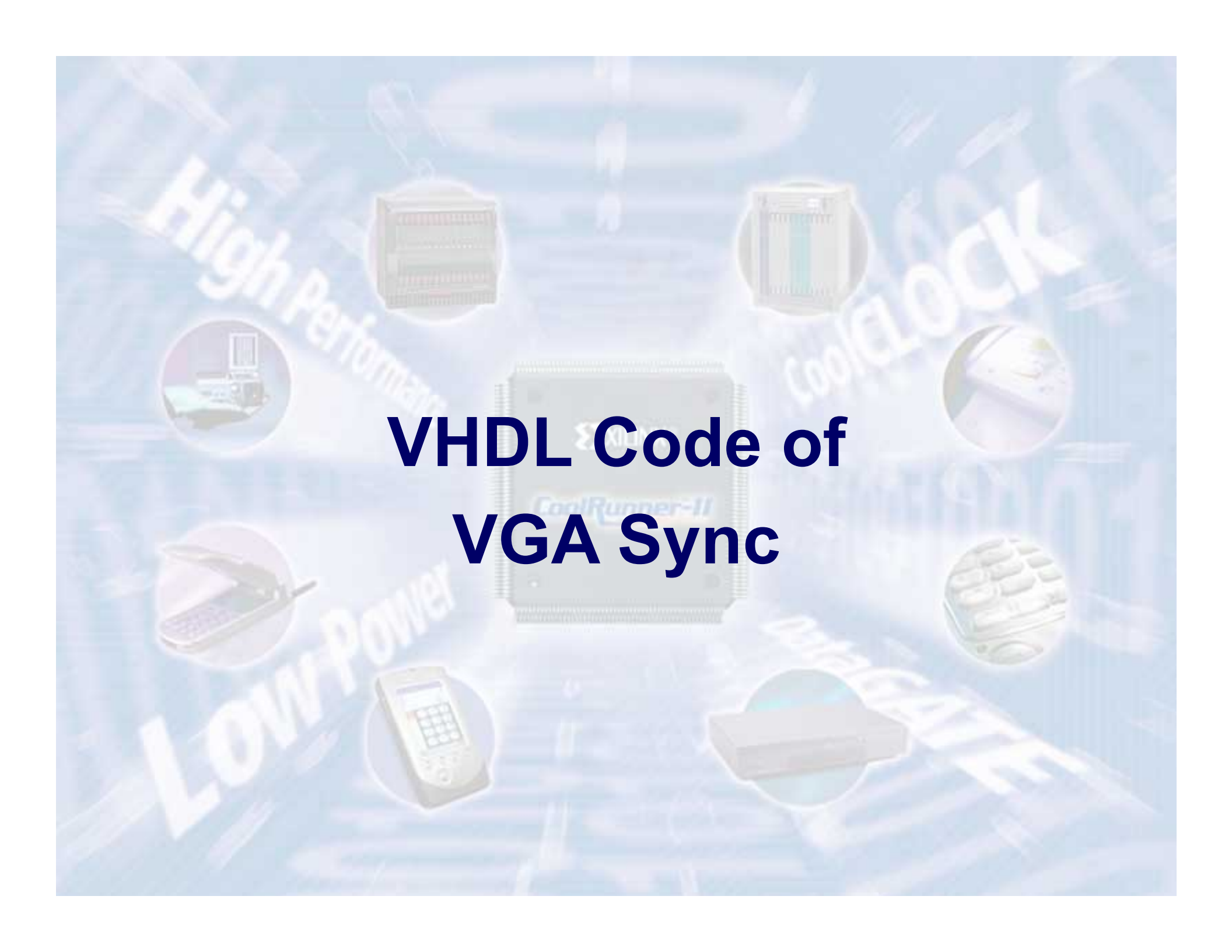The background is a light blue collage featuring various electronic components and text. At the center is a large, detailed image of a CoolRunner-II FPGA chip. Surrounding it are several circular insets containing images of other electronic parts: a multi-pin connector, a small circuit board, a mobile phone, a keypad, and a small module. Diagonal text elements like 'High Performance', 'CoolClock', 'Low Power', and 'DataCache' are scattered across the background.

VHDL Code of VGA Sync

Assumptions

- 50 MHz clock
 - => 2 clock cycles per pixel
 - => p_tick generated every second clock period
used as an enable for the horizontal counter

VHDL Code of VGA Sync (1)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity vga_sync is
  port(
    clk, reset: in std_logic;
    hsync, vsync: out std_logic;
    video_on, p_tick: out std_logic;
    pixel_x, pixel_y: out std_logic_vector (9 downto 0)
  );
end vga_sync;
```

VHDL Code of VGA Sync (2)

architecture arch of vga_sync is

-- VGA 640-by-480 sync parameters

constant HD: integer:=640; --horizontal display area

constant HF: integer:=16 ; --h. front porch

constant HR: integer:=96 ; --h. retrace

constant HB: integer:=48 ; --h. back porch

constant VD: integer:=480; --vertical display area

constant VF: integer:=10; --v. front porch

constant VR: integer:=2; --v. retrace

constant VB: integer:=33; --v. back porch

VHDL Code of VGA Sync (3)

```
-- mod-2 counter
signal mod2_reg, mod2_next: std_logic;

-- sync counters
signal v_count_reg, v_count_next: unsigned(9 downto 0);
signal h_count_reg, h_count_next: unsigned(9 downto 0);

-- output buffer
signal v_sync_reg, h_sync_reg: std_logic;
signal v_sync_next, h_sync_next: std_logic;

-- status signal
signal h_end, v_end, pixel_tick: std_logic;
```

VHDL Code of VGA Sync (4)

```
process (clk, reset)
begin
    if reset='1' then
        mod2_reg <= '0';
        v_count_reg <= (others=>'0');
        h_count_reg <= (others=>'0');
        v_sync_reg <= '0';
        h_sync_reg <= '0';
    elsif (clk'event and clk='1') then
        mod2_reg <= mod2_next;
        v_count_reg <= v_count_next;
        h_count_reg <= h_count_next;
        v_sync_reg <= v_sync_next;
        h_sync_reg <= h_sync_next;
    end if;
end process;
```

VHDL Code of VGA Sync (5)

```
-- mod-2 circuit to generate 25 MHz enable tick
mod2_next <= not mod2_reg;

-- 25 MHz pixel tick
pixel_tick <= '1' when mod2_reg='1' else '0';

-- status
h_end <= -- end of horizontal counter
    '1' when h_count_reg=(HD+HF+HR+HB-1) else --799
    '0';
v_end <= -- end of vertical counter
    '1' when v_count_reg=(VD+VF+VR+VB-1) else --524
    '0';
```

VHDL Code of VGA Sync (6)

```
-- mod-800 horizontal sync counter
process (h_count_reg, h_end, pixel_tick)
begin
    if pixel_tick='1' then -- 25 MHz tick
        if h_end='1' then
            h_count_next <= (others=>'0');
        else
            h_count_next <= h_count_reg + 1;
        end if;
    else
        h_count_next <= h_count_reg;
    end if;
end process;
```

VHDL Code of VGA Sync (7)

```
-- mod-525 vertical sync counter
process (v_count_reg, h_end, v_end, pixel_tick)
begin
    if pixel_tick='1' and h_end='1' then
        if (v_end='1') then
            v_count_next <= (others=>'0');
        else
            v_count_next <= v_count_reg + 1;
        end if;
    else
        v_count_next <= v_count_reg;
    end if;
end process;
```

VHDL Code of VGA Sync (8)

```
-- horizontal and vertical sync, buffered to avoid glitch
h_sync_next <=
    '0' when (h_count_reg >= (HD+HF))           --656
        and (h_count_reg <= (HD+HF+HR-1)) else --751
    '1';
v_sync_next <=
    '0' when (v_count_reg >= (VD+VF))           --490
        and (v_count_reg <= (VD+VF+VR-1)) else --491
    '1';
-- video on/off
video_on <=
    '1' when (h_count_reg<HD) and (v_count_reg<VD) else
    '0';
```

VHDL Code of VGA Sync (9)

```
-- output signal
hsync <= h_sync_reg;
vsync <= v_sync_reg;
pixel_x <= std_logic_vector(h_count_reg);
pixel_y <= std_logic_vector(v_count_reg);
p_tick <= pixel_tick;

end arch;
```

VGA Sync Testing Circuit (1)

```
library ieee;
use ieee.std_logic_1164.all;
entity vga_test is
  port (
    clk, reset: in std_logic;
    sw: in std_logic_vector(2 downto 0);
    hsync, vsync: out std_logic;
    rgb: out std_logic_vector(2 downto 0)
  );
end vga_test;

architecture arch of vga_test is
  signal rgb_reg: std_logic_vector(2 downto 0);
  signal video_on: std_logic;
```

VGA Sync Testing Circuit (2)

```
begin
vga_sync_unit: entity work.vga_sync
    port map(clk=>clk, reset=>reset,
              hsync=>hsync, vsync=>vsync, video_on=>video_on,
              p_tick=>open, pixel_x=>open, pixel_y=>open);
process (clk, reset)
begin
    if reset='1' then
        rgb_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
        rgb_reg <= sw;
    end if;
end process;
rgb <= rgb_reg when video_on='1' else "000";
end arch;
```

Pixel Generation Circuit




High Performance

CoolClock

Low Power

DataCache

VGA Controller – Simplified View

 

Bit-Mapped Pixel Generation Circuit

- Video memory is used to store data to be displayed on the screen
- Each pixel is represented by a memory word holding its color
- Graphics processing circuit continuously updates the screen by writing to the video memory, which is then read by the Pixel Generation Circuit
- Memory needed
 - $640 \cdot 480 = 310$ kbits for a monochrome display
 - $640 \cdot 480 \cdot 3 = 930$ kbits for an 8-color display

Tile-Mapped Pixel Generation Circuit


- Tile = a group of pixels, e.g., 8x8 square of pixels
- The 640x480 pixel-oriented screen becomes an 80x60 tile-oriented screen
- The tile can hold a limited number of patterns, e.g. 32
- For each tile we need to store the number of a displayed pattern (in the range 0..31)
- Tile memory

80•60 tiles/screen • 5 bits/tile \approx 24 kbits

Pattern memory


32 patterns • 64 bits/pattern = 2kbit

Example of a Tile Pattern

 


Object-Mapped Scheme

- RGB signals are generated on the fly based on the values of x and y coordinates (pixel_x, pixel_y)
- Applicable to a limited number of simple objects
- No memory needed

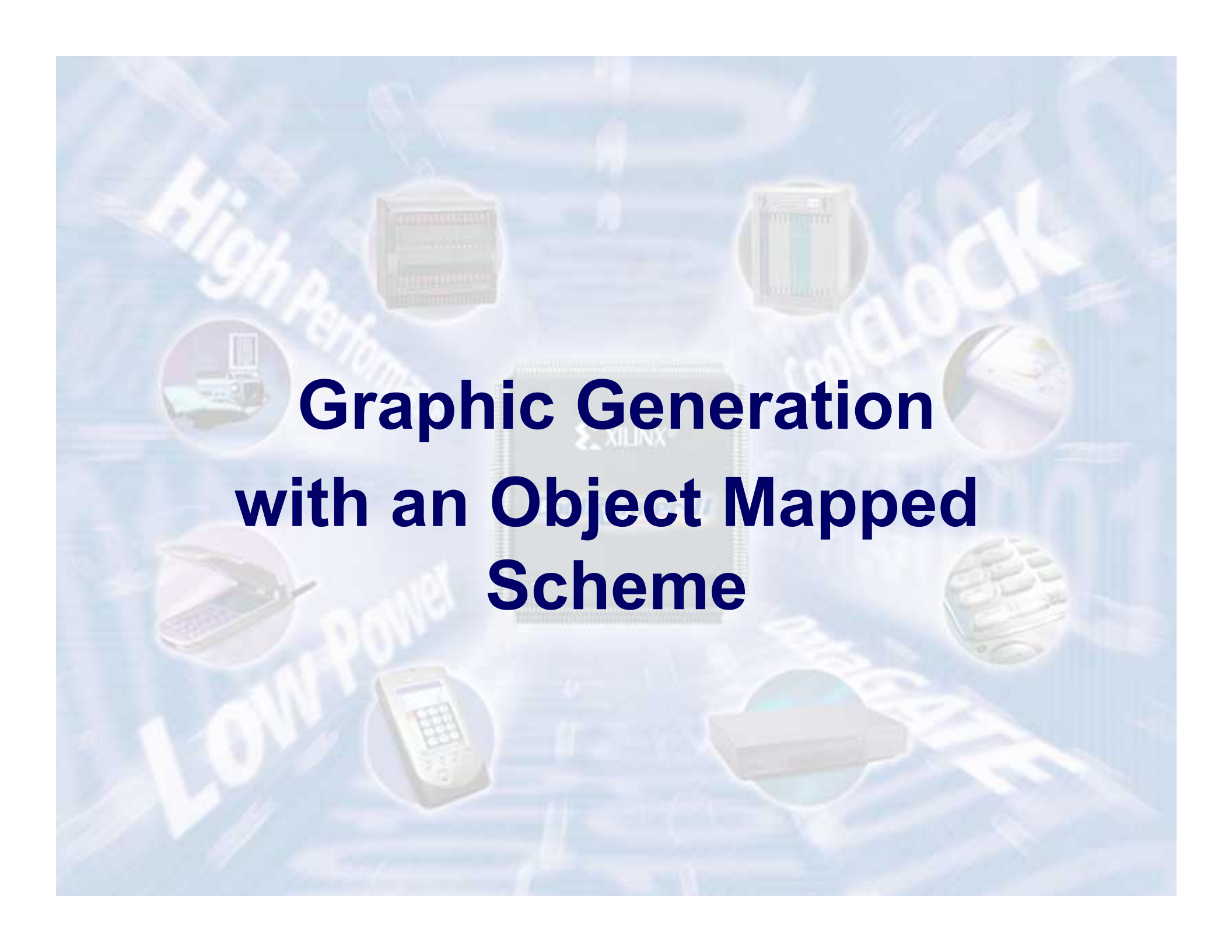
The background is a light blue collage featuring various technology-related icons and text. Icons include a server rack, a circuit board, a mobile phone, a PDA, a keyboard, and a CD-ROM. Text elements include "High Performance", "Low Power", "Data Cache", and "XILINX".

Graphic Generation with an Object Mapped Scheme


Object-Mapped Pixel Generation

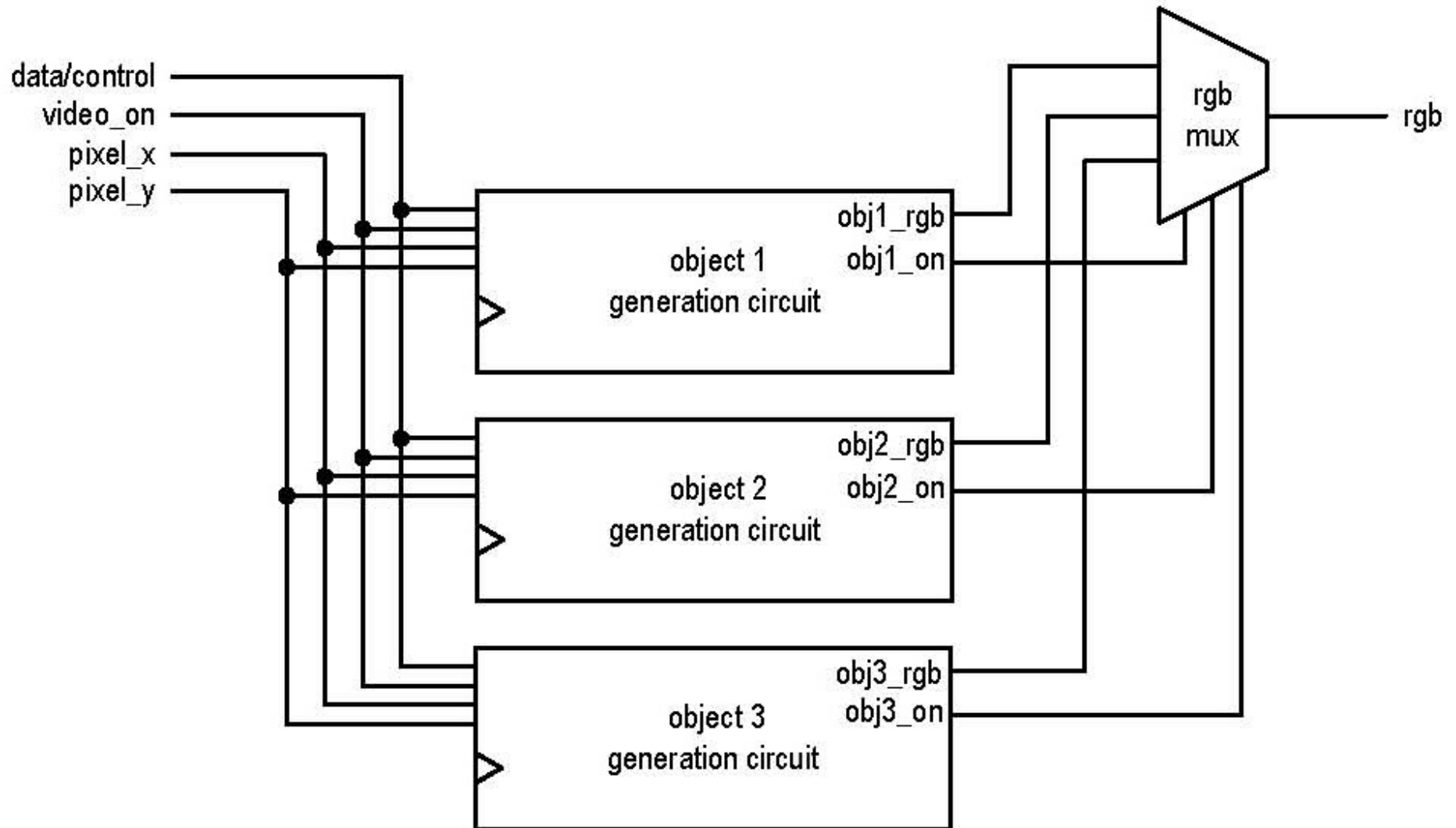

Still Screen of the Pong Game

 

Generation of the Wall Stripe

 


$$32 \leq x \leq 35$$

Generation of the Wall Stripe in VHDL

```
-- wall left, right boundary
constant WALL_X_L: integer:=32;
constant WALL_X_R: integer:=35;

.....
-- pixel within wall
wall_on <=
    '1' when (WALL_X_L<=pix_x) and (pix_x<=WALL_X_R) else
    '0';
-- wall rgb output
wall_rgb <= "001"; -- blue
```

Generation of the Bar (Paddle)

 


$$600 \leq x \leq 603$$

$$204 \leq y \leq 275$$

Generation of the Bar in VHDL

```
constant MAX_X: integer:=640;
constant MAX_Y: integer:=480;
constant BAR_X_L: integer:=600;
constant BAR_X_R: integer:=603;
constant BAR_Y_SIZE: integer:=72;
constant BAR_Y_T: integer:=MAX_Y/2-BAR_Y_SIZE/2; --204
constant BAR_Y_B: integer:=BAR_Y_T+BAR_Y_SIZE-1;
.....
bar_on <=
    '1' when (BAR_X_L<=pix_x) and (pix_x<=BAR_X_R) and
              (BAR_Y_T<=pix_y) and (pix_y<=BAR_Y_B) else
    '0';
bar_rgb <= "010"; --green
```

Generation of the Square Ball

 


$$580 \leq x \leq 587$$

$$238 \leq y \leq 245$$

Generation of the Square Ball in VHDL

```
constant BALL_SIZE: integer:=8;
constant BALL_X_L: integer:=580;
constant BALL_X_R: integer:=BALL_X_L+BALL_SIZE-1;
constant BALL_Y_T: integer:=238;
constant BALL_Y_B: integer:=BALL_Y_T+BALL_SIZE-1;
.....
sq_ball_on <=
    '1' when (BALL_X_L<=pix_x) and (pix_x<=BALL_X_R) and
              (BALL_Y_T<=pix_y) and (pix_y<=BALL_Y_B) else
    '0';
ball_rgb <= "100";  -- red
```

Selection and Multiplexing Circuit

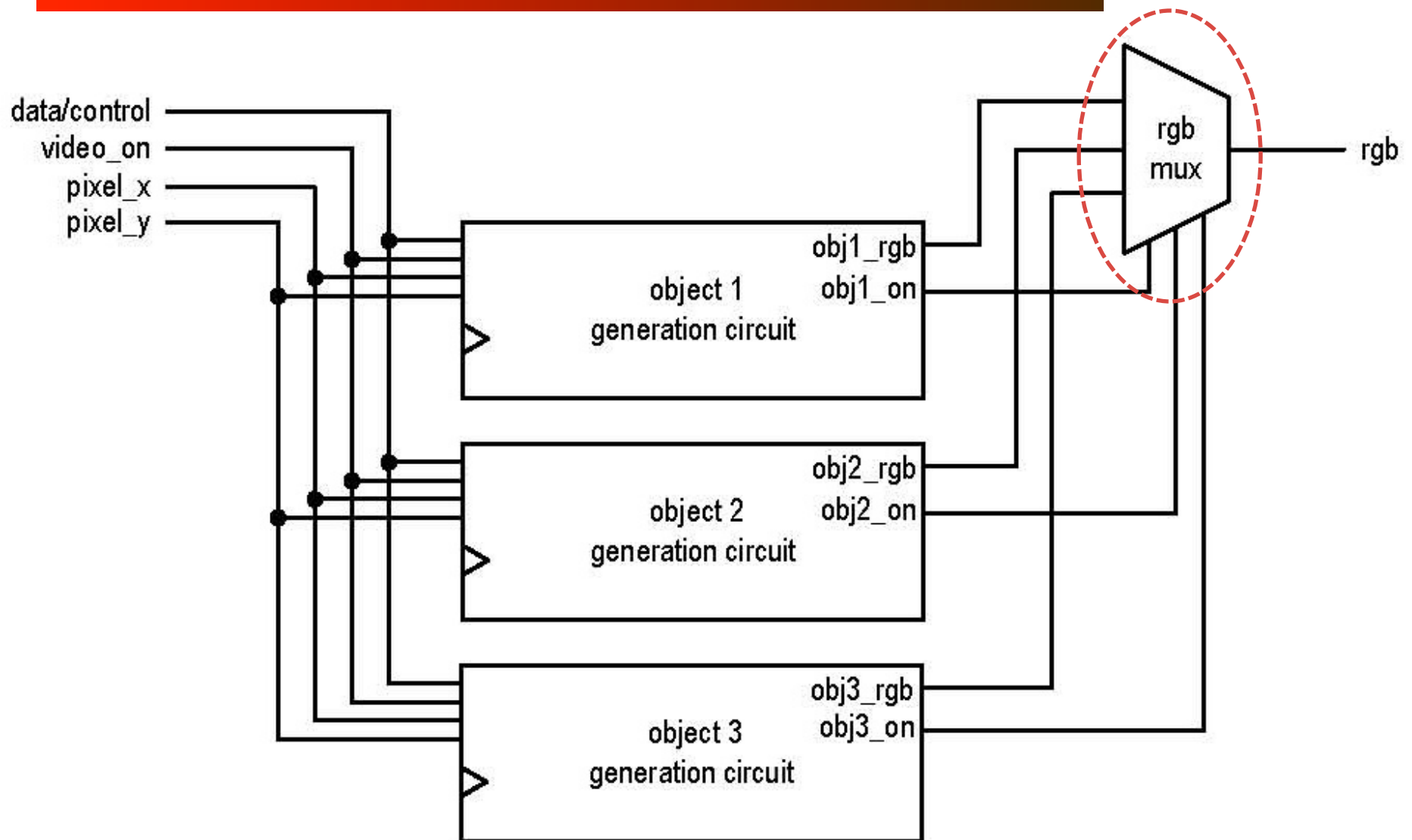

Selection and Multiplexing in VHDL

```
process(video_on, wall_on, bar_on, sq_ball_on, wall_rgb, bar_rgb, ball_rgb)
begin
    if video_on='0' then
        graph_rgb <= "000"; --blank
    else
        if wall_on='1' then
            graph_rgb <= wall_rgb;
        elsif bar_on='1' then
            graph_rgb <= bar_rgb;
        elsif sq_ball_on='1' then
            graph_rgb <= ball_rgb;
        else
            graph_rgb <= "110"; -- yellow background
        end if;
    end if;
end process;
```


The background is a light blue collage featuring various technology-related icons and text. Icons include a server rack, a microprocessor, a mobile phone, a PDA, a CD-ROM, and a hard drive. Text elements include 'High Performance', 'CoolClock', 'Low Power', and 'DataCache'. A central microprocessor is also visible.

Pixel Generation Circuit for the Pong Game Screen

VHDL Code of Pixel Generation (1)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity pong_graph_st is
  port(
    video_on: in std_logic;
    pixel_x, pixel_y: in std_logic_vector(9 downto 0);
    graph_rgb: out std_logic_vector(2 downto 0)
  );
end pong_graph_st;
```

VHDL Code of Pixel Generation (2)

architecture sq_ball_arch of pong_graph_st is

```
-- x, y coordinates (0,0) to (639,479)
signal pix_x, pix_y: unsigned(9 downto 0);
constant MAX_X: integer:=640;
constant MAX_Y: integer:=480;

-----

-- vertical strip as a wall

-----

-- wall left, right boundary
constant WALL_X_L: integer:=32;
constant WALL_X_R: integer:=35;

-----
```

VHDL Code of Pixel Generation (3)

```
-----  
-- right vertical bar
```

```
-----  
-- bar left, right boundary
```

```
constant BAR_X_L: integer:=600;
```

```
constant BAR_X_R: integer:=603;
```

```
-- bar top, bottom boundary
```

```
constant BAR_Y_SIZE: integer:=72;
```

```
constant BAR_Y_T: integer:=MAX_Y/2-BAR_Y_SIZE/2; --204
```

```
constant BAR_Y_B: integer:=BAR_Y_T+BAR_Y_SIZE-1;
```

VHDL Code of Pixel Generation (4)

```
-- square ball
constant BALL_SIZE: integer:=8;
-- ball left, right boundary
constant BALL_X_L: integer:=580;
constant BALL_X_R: integer:=BALL_X_L+BALL_SIZE-1;
-- ball top, bottom boundary
constant BALL_Y_T: integer:=238;
constant BALL_Y_B: integer:=BALL_Y_T+BALL_SIZE-1;

-- object output signals
signal wall_on, bar_on, sq_ball_on: std_logic;

signal wall_rgb, bar_rgb, ball_rgb: std_logic_vector(2 downto 0);
```

VHDL Code of Pixel Generation (5)

```
begin
  pix_x <= unsigned(pixel_x);
  pix_y <= unsigned(pixel_y);

  -----

  -- (wall) left vertical strip

  -----

  -- pixel within wall
  wall_on <=
    '1' when (WALL_X_L<=pix_x) and (pix_x<=WALL_X_R) else
    '0';

  -- wall rgb output

  wall_rgb <= "001"; -- blue
```

VHDL Code of Pixel Generation (6)

```
-----  
-- right vertical bar
```

```
-----  
-- pixel within bar
```

```
bar_on <=
```

```
    '1' when (BAR_X_L<=pix_x) and (pix_x<=BAR_X_R) and  
            (BAR_Y_T<=pix_y) and (pix_y<=BAR_Y_B) else
```

```
    '0';
```

```
-- bar rgb output
```

```
bar_rgb <= "010"; --green
```

VHDL Code of Pixel Generation (7)

```
-----  
-- square ball  
-----
```

```
-- pixel within squared ball
```

```
sq_ball_on <=
```


```
    '1' when (BALL_X_L<=pix_x) and (pix_x<=BALL_X_R) and  
             (BALL_Y_T<=pix_y) and (pix_y<=BALL_Y_B) else
```

```
    '0';
```

```
ball_rgb <= "100";  -- red
```


VHDL Code of Pixel Generation (8)

```
process(video_on, wall_on, bar_on, sq_ball_on, wall_rgb, bar_rgb, ball_rgb)
begin
    if video_on='0' then
        graph_rgb <= "000"; --blank
    else
        if wall_on='1' then
            graph_rgb <= wall_rgb;
        elsif bar_on='1' then
            graph_rgb <= bar_rgb;
        elsif sq_ball_on='1' then
            graph_rgb <= ball_rgb;
        else
            graph_rgb <= "110"; -- yellow background
        end if;
    end if;
end process;
end sq_ball_arch;
```

The background is a light blue collage featuring various electronic components and terms. At the top left, the words "High Performance" are written in a large, white, sans-serif font. At the top right, "CoolClock" is written in a similar font. In the bottom left, "Low Power" is written. In the bottom right, "DataCache" is written. The central text "Displaying a Non-Rectangular Object" is in a bold, dark blue font. Surrounding the text are several circular icons: a server rack, a microprocessor, a desktop computer, a mobile phone, a calculator, and a small electronic device. The overall theme is technology and electronics.

Displaying a Non-Rectangular Object

Option 1: Using Equation of a Circle

- Check whether

$$(x - x_0)^2 + (y - y_0)^2 \leq R^2$$

Option 2: Using Pattern ROM

- First check whether

$$x_0 - R \leq x \leq x_0 + R$$

and


$$y_0 - R \leq y \leq y_0 + R$$

- Then, use

$$x - (x_0 - R) \text{ and } y - (y_0 - R)$$

as an address in the pattern memory

Bit Map of a Circle

 

Bit Map of a Circle in VHDL

```
type rom_type is array (0 to 7) of std_logic_vector(0 to 7);
-- ROM definition
constant BALL_ROM: rom_type :=
(
    "00111100", -- ****
    "01111110", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "01111110", -- *****
    "00111100" -- ****
);
```

VHDL Code of a Ball Generator (1)

```
constant BALL_SIZE: integer:=8; -- 8
-- ball left, right boundary
signal ball_x_l, ball_x_r: unsigned(9 downto 0);
-- ball top, bottom boundary
signal ball_y_t, ball_y_b: unsigned(9 downto 0);

signal rom_addr, rom_col: unsigned(2 downto 0);
signal rom_data: std_logic_vector(7 downto 0);
signal rom_bit: std_logic;
```

VHDL Code of a Ball Generator (2)

```
type rom_type is array (0 to 7) of std_logic_vector(0 to 7);
-- ROM definition
constant BALL_ROM: rom_type :=
(
    "00111100", -- ****
    "01111110", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "11111111", -- *****
    "01111110", -- *****
    "00111100" -- ****
);
```


VHDL Code of a Ball Generator (3)

```
-- pixel within ball
sq_ball_on <=
    '1' when (ball_x_l<=pix_x) and (pix_x<=ball_x_r) and
              (ball_y_t<=pix_y) and (pix_y<=ball_y_b) else
    '0';

-- map current pixel location to ROM addr/col
rom_addr <= pix_y(2 downto 0) - ball_y_t(2 downto 0);
rom_col  <= pix_x(2 downto 0) - ball_x_l(2 downto 0);
rom_data <= BALL_ROM(to_integer(rom_addr));
rom_bit <= rom_data(to_integer(rom_col));
```

VHDL Code of a Ball Generator (4)

```
-- pixel within ball
rd_ball_on <=
    '1' when (sq_ball_on='1') and (rom_bit='1') else
    '0';
-- ball rgb output
ball_rgb <= "100";  -- red
```